

## CHAPTER - ELECTRICITY

### WORKSHEET

1. Calculate the potential difference required across a conductor of resistance  $5\ \Omega$  to make a current of  $1.5\ \text{A}$  flow through it.
2. A torch bulb has  $1\ \Omega$  resistance. It draws a current of  $0.3\ \text{A}$  when glowing from a source of  $3\ \text{V}$ . Calculate the resistance of the bulb when glowing and explain the reason for the difference in resistance.
3. How much current does an electric heater draw from a  $220\ \text{V}$  line, if the resistance of the heater (when hot) is  $50\ \Omega$ ?
4. How much work is done in moving a charge of  $2\ \text{C}$  across two points having a potential difference of  $12\ \text{V}$ ?
5. An incandescent lamp of resistance  $80\ \Omega$  draws a current of  $0.75\ \text{A}$ . Find the line voltage.
6. A current of  $0.2\ \text{A}$  flows through a conductor of resistance  $4.5\ \Omega$ . Calculate the potential difference at the ends of the conductor.
7. A bulb of resistance  $400\ \Omega$  is connected to  $220\ \text{V}$  mains. Calculate the magnitude of current.
8. An electric heater draws a current of  $5\ \text{A}$  when connected to  $220\ \text{V}$  mains. Calculate the resistance of its filament.
9. How much current will an electric bulb draw from a  $220\ \text{V}$  source, if the resistance of the bulb filament is  $1200\ \Omega$ ?
10. The potential difference between the terminals of an electric heater is  $60\ \text{V}$  when it draws a current of  $4\ \text{A}$  from the source. Calculate the resistance of electric heater. What happens to current if potential difference is doubled?

**Answer:**

1. Resistance of the conductor,  $R = 5 \Omega$

Required current,  $I = 1.5 \text{ A}$

If  $V$  is the potential difference required across the conductor, then

$$V = IR = 1.5 \times 5 = 7.5 \text{ V}$$

2. Potential difference,  $V = 3 \text{ volt}$

Current through the bulb when glowing,  $I = 0.3 \text{ A}$

Resistance of the bulb when glowing,  $R = \frac{V}{I} = \frac{3}{0.3} = 10 \Omega$

The resistance of the filament of the bulb increases from  $1 \Omega$  to  $10 \Omega$  (when it becomes hot and glows) because of an increase in its temperature.

3. Potential difference,  $V = 220 \text{ V}$

Resistance of the heater,  $R = 50 \Omega$

Using ohm's law,  $I = \frac{V}{R} = \frac{220}{50} = 4.4 \text{ A}$

4.  $W = QV = 2\text{C} \times 12\text{V} = 24 \text{ J}$

5.  $V = IR = 0.75 \times 80 = 60 \text{ V}$

6.  $V = IR = 0.2 \times 4.5 = 0.9 \text{ V}$

$$7. I = V/R = 220/400 = 0.55 \text{ A}$$

$$3. R = V/I = 220/5 = 44 \Omega$$

$$3. I = \frac{V}{R} = \frac{220\text{V}}{1200\Omega} = 0.18 \text{ A}$$

$$2. \text{ Resistance of the electric heater, } R = \frac{V}{I} = \frac{60\text{V}}{4\text{A}} = 15 \Omega$$

Changed potential difference  $V' = 120 \text{ V}$

$$\text{Changed current, i.e., } I' = \frac{V'}{R} = \frac{120\text{V}}{15\Omega} = 8 \text{ A}$$

Since  $R$  remains the same, by doubling the potential difference, the current is also doubled, i.e., becomes  $8 \text{ A}$  as  $I \propto V$ .